

# Extra Questions from Lab 2

Alex Hiller

September 17, 2018

## Contents

# 1 Balanced Load, Lagging Power Factor

## 1.1 Question 5

*Compare your results in Table 2.1 and Table 2.5 and give your comments.*

Quantity	Table 2.1	Measured in Lagging	Difference (%)
$ V_{AN} $	150.0 V	149.9 V	0.067
$ V_{AB} $	259.8 V	262.8 V	1.142
$ V_{BC} $	259.8 V	264.6 V	1.814
$ I_A $	1.778 A	1.790 A	0.671
$ I_B $	1.778 A	1.802 A	1.332
$ I_C $	1.778 A	1.810 A	1.768
$P_A$	225 W	450 W	50.00
$P_C$	225 W	235 W	4.255
$P$	450 W	685 W	34.31
$Q$	0 var	372.39 var	$\infty$
$pf_A$	1 (?)	0.998	0.200
$pf_C$	1 (?)	0.508	96.85

The voltages and currents were similar to those predicted before the lab. But parameters related to power were either poorly measured or poorly predicted (poorly predicted is more likely).

Because the team assumed a positive phase sequence in experimentation, wattmeter measurements were made over the wrong phase. It is listed as  $C$  phase, but because of the negative phase sequence of the bench, it is actually  $B$  phase. Because of this, our two-wattmeter-method is very likely wrong and the power measurements would ideally be redone.

## 2 Balanced Load, Unity Power Factor

### 2.1 Question 6

*Compare your results in Table 2.2 and Table 2.6 and give your comments.*

Quantity	Table 2.2	Measured in Unity	Difference (%)
$ I_A $	1.5 A	1.581 A	5.122
$ I_B $	1.5 A	1.586 A	5.422
$ I_C $	1.5 A	1.599 A	6.191
$P_A$	337.5 W	341 W	1.026
$P_C$	337.5 W	363 W	7.025
$P$	675.0 W	704 W	4.119
$Q$	0 var	-38.11 var	$\infty$

The currents  $I_B$  and  $I_C$  were not in the original Table 2.2 but assumedly they would also be of magnitude 1.5 Amperes in a balanced load with unity power factor.

Measurements were very close to predicted, however measuring the percentage difference to a quantity that should be zero gives an infinite difference, though only -38 var is a small enough amount to be due to imperfect elements used in the experiment (as opposed to the ideal ones used in the calculations).

### **3   Balanced Load, Leading Power Factor**



#### **3.1   Nil**

All questions were answered in the provided lab document.

## 4 Unbalanced Three-Wire Circuit

### 4.1 Question 6

Use a graphical method for determining  $V_{AO}$ ,  $V_{BO}$  and  $V_{CO}$  from  $|V_{AO}|$ ,  $|V_{BO}|$  and  $|V_{CO}|$  and compare results with those of Table 2.4

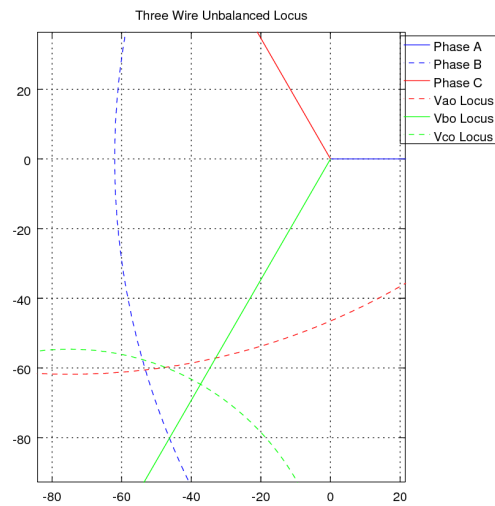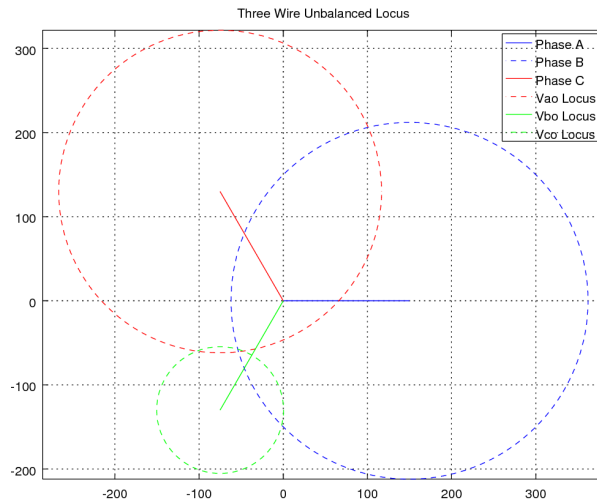

Looking at the loci closely, it can be seen that  $V_{ON}$  can be approximated graphically by:

$$\|V_{ON}\| = \sqrt{(-50)^2 + (-60)^2} = 78.102V$$

$$\theta_{von} = 180 + \tan^{-1} \left( \frac{-60}{-50} \right) = 230.194^\circ$$

Graphical calculations:

$$V_{AO} = V_{AN} - V_{ON} = 150\angle 0^\circ - 78.102\angle 230.194^\circ = 208.806\angle 16.699^\circ$$

$$V_{BO} = V_{BN} - V_{ON} = 150\angle 120^\circ - 78.102\angle 230.194^\circ = 191.541\angle 97.499^\circ$$

$$V_{CO} = V_{CN} - V_{ON} = 150\angle 240^\circ - 78.102\angle 230.194^\circ = 74.2404\angle -109.67^\circ$$

Value	Table 2.4	Measured	Graphical
$V_{on}$	214.337 $\angle$ 127.134	-	78.102 $\angle$ 230.194
$V_{ao}$	327.502 $\angle$ -31.4	$\ 212.7\ $	208.806 $\angle$ 16.699 $^\circ$
$V_{bo}$	68 $\angle$ -36.98	$\ 75.4\ $	191.541 $\angle$ 97.499 $^\circ$
$V_{co}$	225 $\angle$ 76.04	$\ 192.7\ $	74.2404 $\angle$ -109.67 $^\circ$

## 4.2 Question 8

*Give your comments and conclusions.*

It would seem that the calculations were all done assuming positive phase sequence, but the bench itself instead had negative phase sequence. This can be deduced from the above table in the interchanged magnitudes of the  $B$  and  $C$  line.

Besides this experimental mishap, it can be seen that an unbalanced three phase circuit can give widely varying circuit parameters. Even just slight change in parameters at the load can cause large variations between phases.

## 5 Unbalanced Four-Wire Circuit

### 5.1 Question 6

*Use a phasor diagram to determine the expected value of  $|I_{ON}|$  and compare this to the measured value.*

Value	Measured (Absolute Value)	Graphical
$I_O$	1.688	Not Performed
$I_{AO}$	0.904	Not Performed
$I_{BO}$	1.516	Not Performed
$I_{CO}$	1.528	Not Performed

### 5.2 Question 8

*Give your comments and conclusions.*